

TSN1101

Computer Architecture and Organization

Section A (Digital Logic Design)

Lecture A-06

Sequential Logic Circuits – Flip-flops

TOPIC COVERAGE IN THE LECTURE

- ❑ Sequential Logic Circuits
 - Synchronous Vs Asynchronous
- ❑ Latches Vs Flip-flops
- ❑ Types of Latches
 - S-R Latch / S'-R' Latch
 - Gated S-R Latch
 - Gated D Latch
- ❑ Types of Flip-flops
 - Clocked/Edge Triggered
 - ❑ S-R Flip-flop
 - ❑ J-K Flip-flop
 - ❑ D Flip-flop
 - ❑ T Flip-flop
- ❑ Flip-flops with Asynchronous Inputs
- ❑ Finite State Machines
 - Mealy Vs Moore Models

Sequential Logic Circuits


- * Introduction
- * Asynchronous Sequential Circuits
- * Synchronous Sequential Circuits

Sequential Logic Circuits

- Introduction

- A Sequential logic circuit consists of combinational logic gates and storage elements.
- Outputs at any time are determined from the external inputs and current state of storage elements.

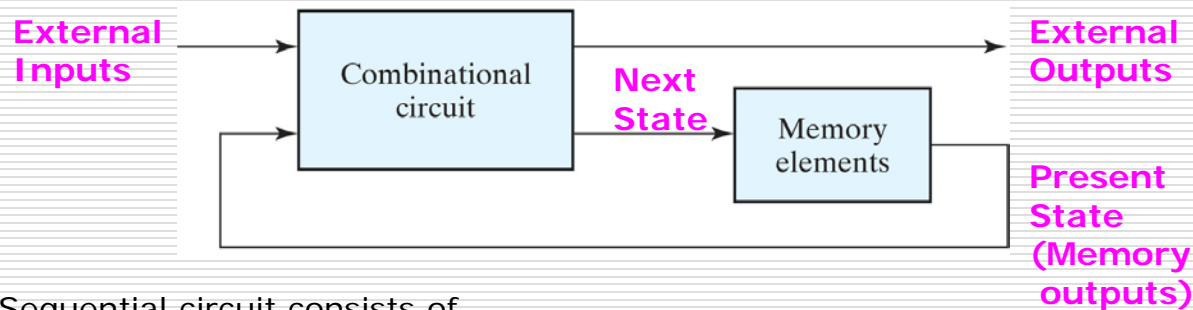Block Diagram of a Sequential Logic Circuit



- A Sequential circuit consists of
 - Memory elements: Latches or Flip-Flops
 - Combinational Logic Circuit:
 - To implement multiple-output logic function
 - External Inputs are signals from the external environment
 - Present State are signals from storage elements
 - External outputs are signals to the outside environment
 - Next State are inputs to storage elements.

Sequential Logic Circuits


- Classification

- ❑ Classification of sequential circuits depends on the times at which memory elements look into their inputs and change their state.
- ❑ **Asynchronous Sequential Circuit**
 - Behavior depends upon input signals at any instant of time and the order in which inputs change
 - Storage elements used are time-delay devices
 - Can be regarded as combinational circuit with feedback
 - May become unstable at times because of feedback among logic gates
 - ❑ can cause difficulties to the designer.
- ❑ **Synchronous Sequential Circuit/Clocked Sequential Circuit**
 - Behavior defined from knowledge of its signals that affect storage elements only at discrete instances of time
 - Synchronization achieved by clock generator which provides clock pulses.
 - Storage elements used are flip-flops
 - ❑ A flip-flop is a binary storage device capable of storing one bit of information.
 - No instability problems

Sequential Logic Circuits

- Synchronous sequential circuit

 Block Diagram of a synchronous (clocked) Sequential Logic Circuit



(a) Block diagram

- The outputs can come from
 - Combinational circuit or
 - flip-flops or
 - both
- Flip-flops receive the inputs from
 - Combinational circuit
 - Clock signal with pulses that occur at fixed time intervals
- The state of flip-flops can change only during clock pulse transition



(b) Timing diagram of clock pulses

Latches

- * Latches Vs Flip-flops
- * Basic S-R Latch using
 - NAND Gates
 - NOR Gates
- * Gated S-R Latch using
 - NAND Gates
 - AND and NOR Gates
- * Gated D Latch using
 - NAND Gates
 - AND, NOR and inverter Gates


Latches Vs Flip-flop

Similarity:

- * Both are bistable multivibrators (having two stable states)

Difference:

 - * Latch does not have clocking source input, while flip-flop has.
 - Latch change the state immediately when the input changes




- Flip-flop waits for the clock signal before changing state.



Latches

 
- A latch is a bistable memory device that can store one bit ('0' or '1') of data.
- It is the simplest possible memory element



Basic \bar{S} – \bar{R} Latch

- Using NAND Gates

 Logic Diagram for active-LOW input \bar{S} - \bar{R} ' NAND Latch




- Active-LOW input \bar{S} - \bar{R} ' latch is formed with **two cross-coupled NAND gates**.
- Output of each gate is connected to an input to the opposite gate, producing a feedback.

Truth table for active-LOW input \bar{S} - \bar{R} ' Latch

INPUTS		OUTPUTS		Output State / COMMENT
\bar{S}	\bar{R}	Q	\bar{Q}	
1	1	NC	NC	No change (HOLD) Latch remains at previous state.
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
0	0	1	1	Invalid Condition/Forbidden


Logic Symbol

 

Basic \overline{S} – \overline{R} Latch

- Using NAND Gates (Operation)

 
Active-LOW input S'-R' NAND Latch with two possible resting states when **SET=RESET=1**



Basic \overline{S} – \overline{R} Latch

- Using NAND Gates (Operation)

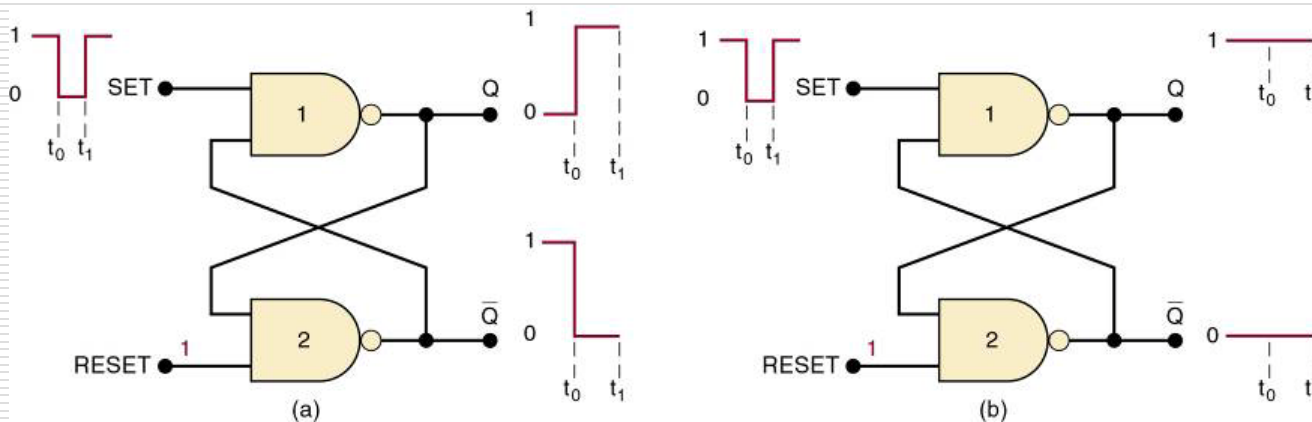Active-LOW input S'-R' NAND Latch when **SET=0** and **CLEAR=1**




Pulsing the SET input to the 0 state (a) $Q = 0$ prior to SET pulse. (b) $Q = 1$ prior to SET pulse.

In both cases, Q ends up HIGH.

Basic \overline{S} – \overline{R} Latch

- Using NAND Gates (Operation)

 Active-LOW input \overline{S} '- \overline{R} ' NAND Latch when **SET=1 and CLEAR=0**



Pulsing the RESET input to the 0 state (a) $Q = 0$ prior to RESET pulse. (b) $Q = 1$ prior to RESET pulse.

In both cases, Q ends up LOW.

Basic \overline{S} – \overline{R} Latch


- Using NAND Gates (Summary)

- **SET = 1, RESET = 1**—Normal **resting state**, outputs remain in state they were in prior to input.
- **SET = 0, RESET = 1**—Output will go to $Q = 1$ and remains there, even after SET returns HIGH.
 - Called **setting** the latch.
- **SET = 1, RESET = 0**—Will produce $Q = 0$ LOW and remains there, even after RESET returns HIGH.
 - Called **clearing or resetting** the latch.
- **SET = 0, RESET = 0**—Tries to set and clear the latch at the same time, and produces output that is unpredictable, and this input condition should not be used - **Forbidden**

Basic \overline{S} – \overline{R} Latch

- Using NAND Gates (Example)

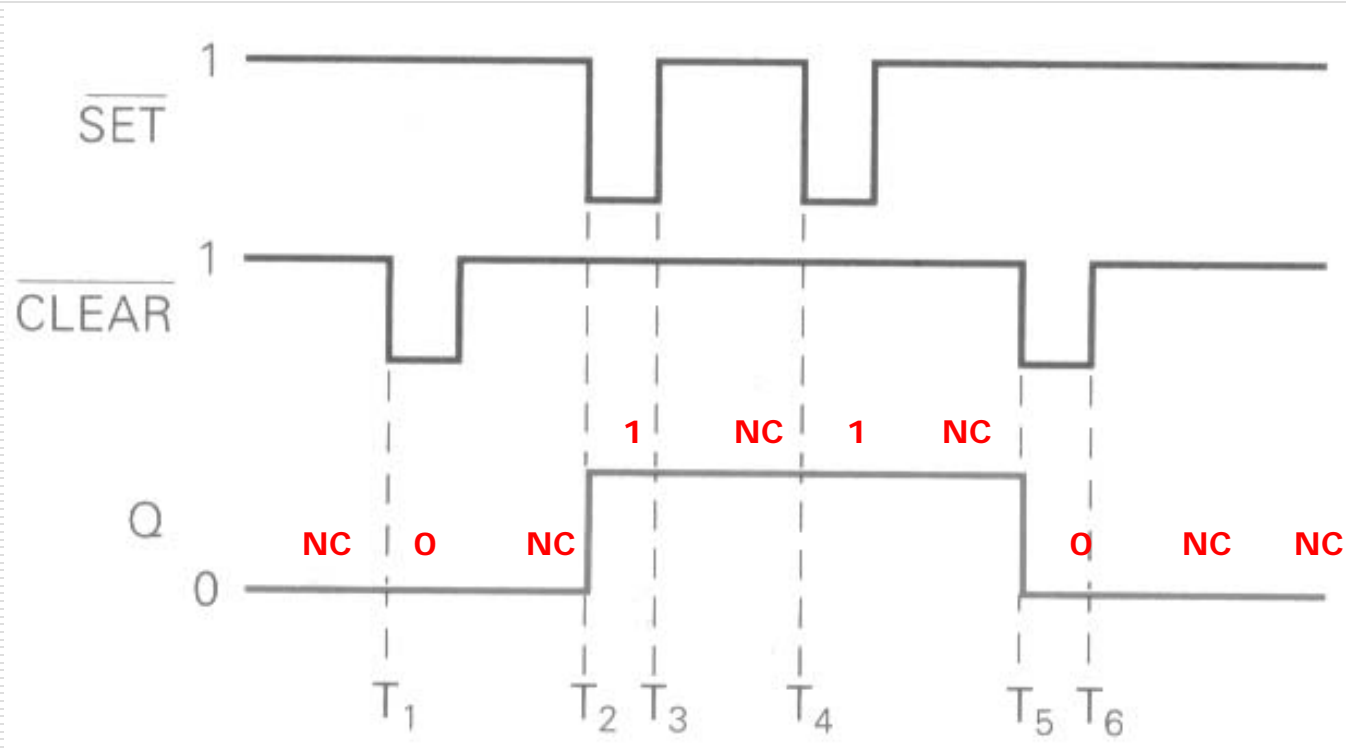
Assuming $Q = 0$ initially, and determine the Q waveform for the NAND latch.



Basic S-R Latch

- Using NOR Gates

 Logic Diagram for active-HIGH input S-R NOR Latch




- Active-HIGH input S-R latch is formed with **two cross-coupled NOR gates**.
- Output of each gate is connected to an input to the opposite gate, producing a feedback.

Truth table for active-HIGH input S-R Latch

INPUTS		OUTPUTS		COMMENT
S	R	Q	Q'	
0	0	NC	NC	No change (Hold) Latch remains at previous state.
1	0	1	0	Latch SET
0	1	0	1	Latch RESET
1	1	0	0	Invalid Condition/ Forbidden

Logic Symbol

 

Basic S–R Latch


- Using NOR Gates (Analysis - Summary)

- The analysis of a S-R latch is described as follows:
 - $S = 0$ and $R = 0$: Q will remain in prior state (**HOLD mode**) . It has no effect to the output. It works in HOLD (no change) mode of operation.
 - $S = 1$ and $R = 0$: it works in **SET mode** of operation, Q will set to 1.
 - $S = 0$ and $R = 1$: it works in **RESET mode** of operation. Q will reset to 0.
 - $S = 1$ and $R = 1$: this is an unexpected condition, because the two outputs try to set and reset at the same time. It is **forbidden mode**.
-

Basic S-R Latch

- Using NOR Gates (Example)

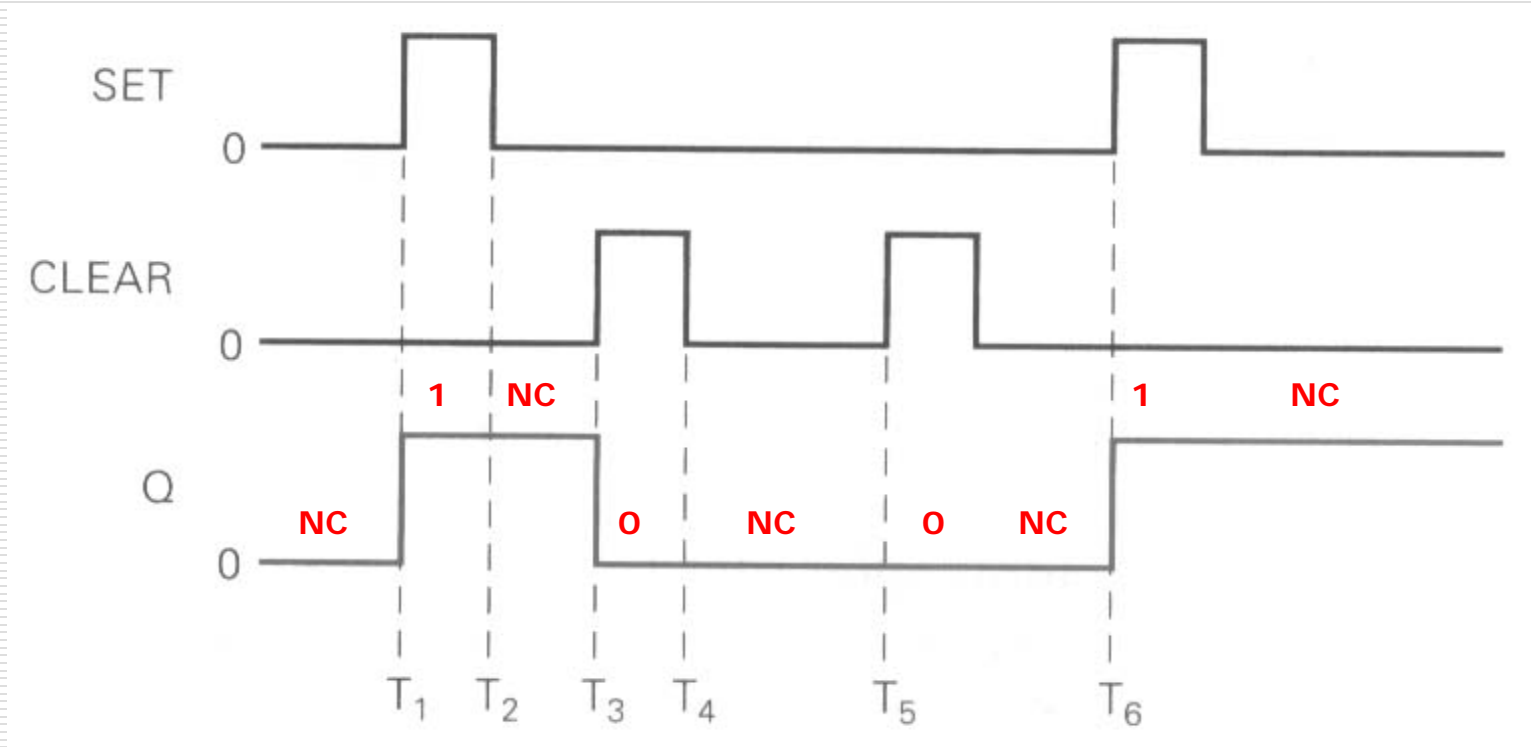Assuming that $Q = 0$ initially, determine the Q waveform for the NOR latch.




Gated S-R Latch

- Using NAND Gates

- A gated latch is a variation on the basic latch.
- The gated latch has an additional input, called enable (EN) that must be HIGH in order for the latch to respond to the S and R inputs.

Example: Show the Q output with relation to the input signals. Assume Q starts LOW.

Logic Diagram for Gated S-R Latch

 


Solution:



Gated S-R Latch

- Using NOR and AND Gates

 Logic Diagram for Gated S-R Latch (with NOR and AND gates)



- When the control input signal (C) is 0, the outputs of the two AND gates are forced to 0, signals applied to the S and R inputs will not affect the cross-coupled NOR latch circuit.

- Hence the circuit behaves as though S and R were both 0, latching the Q and Q' outputs in their last states.

- When the control input signal (C) is activated (1), signals applied to the S and R inputs can affect the cross-coupled NOR latch circuit.

- The gated S-R latch will act like a normal S-R latch.

- Using NOR and AND Gates (Truth Table)

Gated SR latch

- Active HIGH (NOR)


Gated S-R Latch

- Using NOR and AND Gates (Example)

Determine the Q and \bar{Q} output waveform if the inputs shown below are applied to an active-HIGH gated S-R latch that is initially RESET.

(EN=C) is 0,
therefore
outputs are NC

Solution:

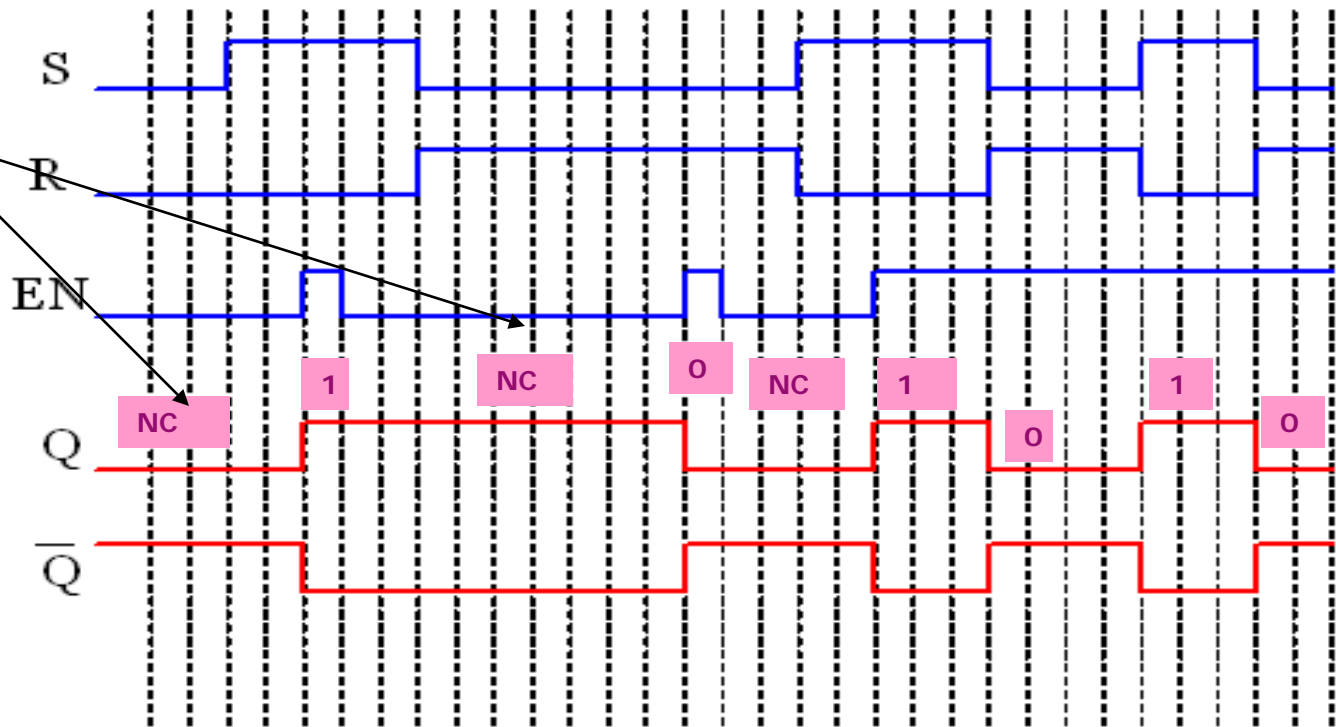


Gated D Latch


- Using NAND Gates

The difference between gated D latch and gated S-R latch is that it has only one input.

 - The D latch is constructed from a gated S-R latch, with an inverter added to make R input as the complement (inverse) of S input.



(a) Logic diagram

 

(b) Logic symbol

Logical Operation:


When D input is HIGH and the EN input is HIGH, the latch will SET.

When D input is LOW and the EN input is HIGH, the latch will RESET

In short, Q output follows the D input when EN is HIGH

Gated D Latch

- Using NOR, AND Gates and inverter

 

Gated D Latch

- Truth Table

Truth table for Gated D Latch

INPUTS		OUTPUTS		COMMENTS
<i>EN</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>	
0	0	NC	NC	No Change
0	1	NC	NC	No Change
1	0	0	1	Latch RESET
1	1	1	0	Latch SET

- As with the gated S-R latch, the D latch will not respond to a signal input if the enable input (EN) is LOW (0). it simply stays latched in its last state (NC)
 - However when the enable input (EN) is HIGH (1), then the Q output follows the D input as long as the control input remains logic 1.
-

Flip-flops


- * Clock Signals and Clocked Flip-flops
 - PGT and NGT
- * Clocked S-R Flip-flop
- * Clocked J-K Flip-flop
- * Clocked D Flip-flop
- * Clocked T Flip-flop
- * Flip-flops – Summary
 - Characteristic Tables, Characteristic equations and Excitation Tables
- * Asynchronous Inputs
- * Flip-flop Applications- Examples

Clock Signals and Clocked Flip-Flops

- Introduction

- The clock signal is a rectangular pulse train or square wave.
 - Positive going transition (PGT)—clock pulse goes from 0 to 1.
 - Negative going transition (NGT)—clock pulse goes from 1 to 0.

Transitions are also called *edges*.

 


Clock Signals and Clocked Flip-Flops


- Introduction

- Clocked FFs change state on one or the other clock transitions.
 - Clock inputs can be labeled as CLK, CK, or CP.

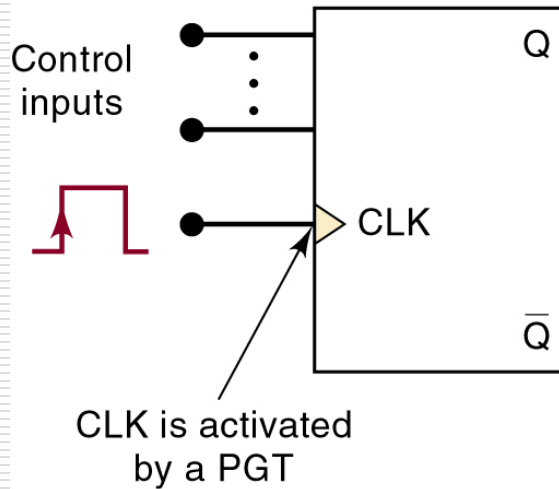A small triangle at the CLK input indicates that the input is activated with a PGT.




 
A bubble and a triangle indicates that the CLK input is activated with a NGT.



Clock Signals and Clocked Flip-Flops

- Introduction

 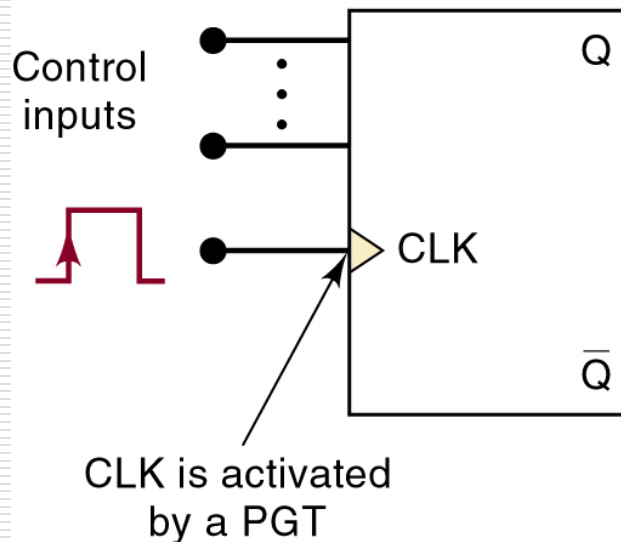- Control inputs have an effect on the output only at the active clock transition (NGT or PGT)—also called synchronous control inputs.
- The control inputs get the outputs ready to change, but the change is not triggered until the CLK edge.




Clocked S-R Flip-Flop

- The S and R inputs are synchronous *control* inputs, which control the state the FF will go to when the clock pulse occurs.
 - The CLK input is the **trigger** input that causes the FF to change states according to the S and R inputs.
 - SET-RESET (or SET-CLEAR) FF will change states at positive- or negative-going clock edges.
-

Clocked S-R Flip-Flop

- Positive Edge Triggering

 A clocked S-R flip-flop triggered by the positive-going edge of the clock signal



Inputs			Output
S	R	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous


Q_0 is output level prior to ↑ of CLK.
↓ of CLK produces no change in Q.

The S and R inputs control the state of the FF in the same manner as described earlier for the **NOR** gate latch, but the FF does *not* respond to these inputs *until* the occurrence of the PGT of the clock signal.

Clocked S-R Flip-Flop

- Positive Edge Triggering (Timing Diagram)

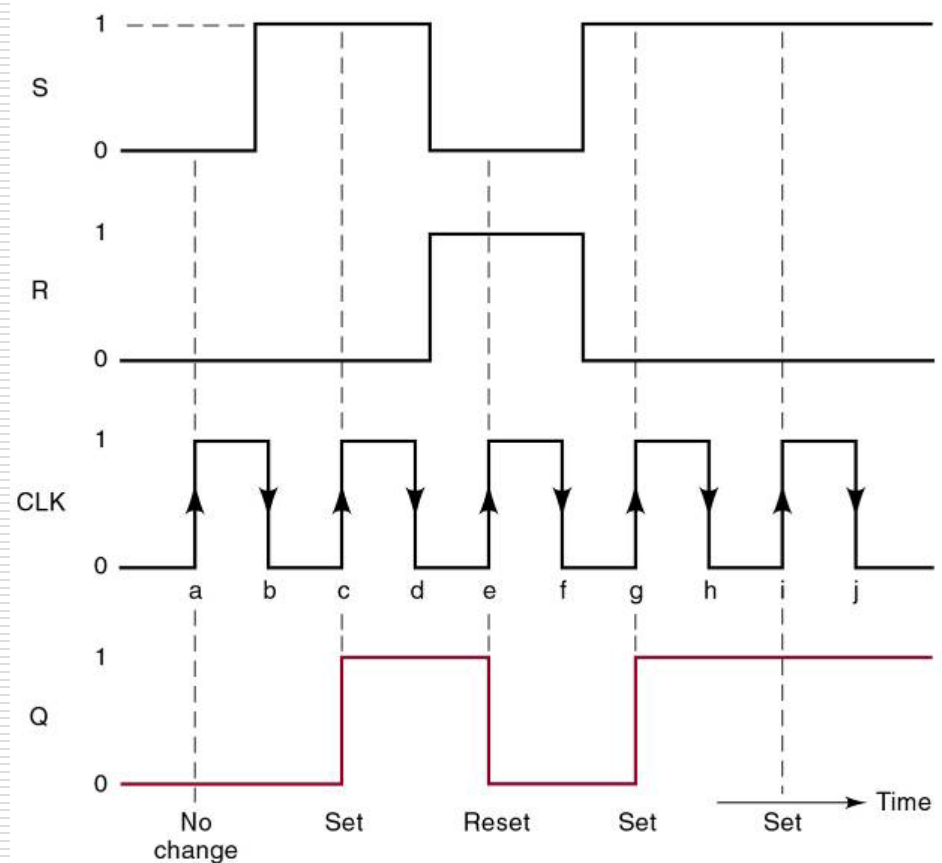
Waveforms of the operation of a clocked S-R flip-flop triggered by the positive-going edge of a clock pulse.



Clocked S-R Flip-Flop

- Negative Edge Triggering

 A clocked S-R flip-flop triggered by the negative-going edge of the clock signal.




Inputs			Output
S	R	CLK	Q
0	0	↓	Q_0 (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	Ambiguous

Both positive-edge and negative-edge triggering FFs are used in digital systems.

Clocked S-R Flip-Flop

- Logic Diagram

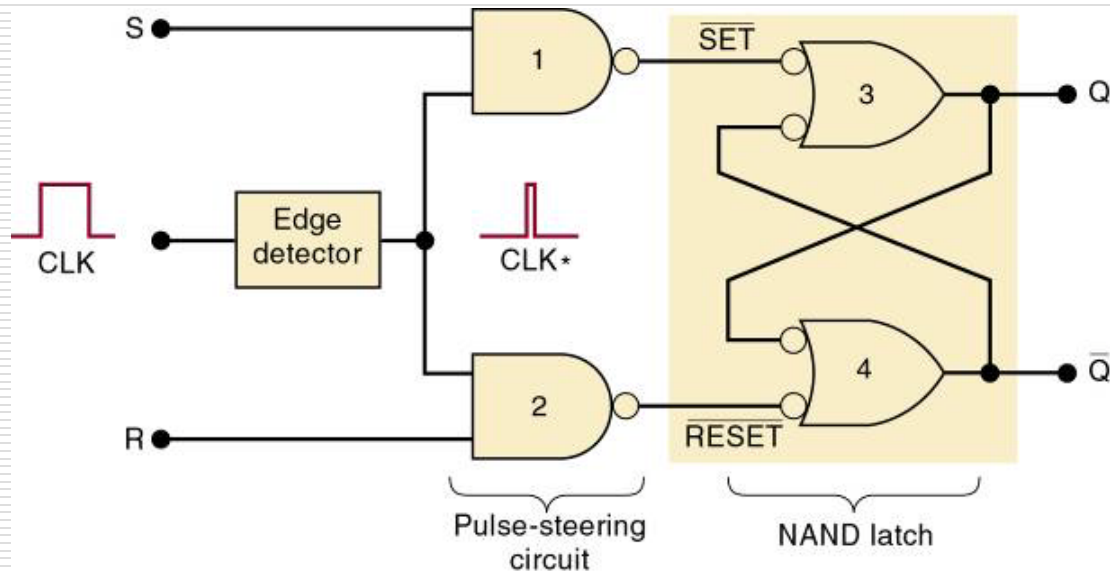


- An edge-triggered S-R flip-flop circuit features:
 - A basic **NAND** gate latch formed by **NAND-3** and **NAND-4**.
 - A **pulse-steering circuit** formed by **NAND-1** and **NAND-2**.
 - An **edge-detector circuit**.

Clocked S-R Flip-Flop

- Logic Diagram (Edge Detector Circuit)

 - Implementation of edge-detector circuits used in edge-triggered flip-flops:
(a) PGT; (b) NGT.



The duration of the CLK^* pulses is typically 2–5 ns.


Clocked J-K (Jack-Kilby) Flip-Flop

- ❑ Operates like the S-R FF.
 - J is SET, K is CLEAR.
 - ❑ When J and K are both HIGH, output is toggled to the opposite state.
 - Can use either positive going or negative going clock trigger.
 - ❑ Much more versatile than the S-R flip-flop, as it has no ambiguous states.
 - Has the ability to do everything the S-R FF does, plus operates in toggle mode.
-


Clocked J-K Flip-Flop

- Positive Edge Triggering

 Clocked J-K flip-flop that responds only to the positive edge of the clock.




J	K	CLK	Q
0	0	\uparrow	Q_0 (no change)
1	0	\uparrow	1
0	1	\uparrow	0
1	1	\uparrow	\bar{Q}_0 (toggles)

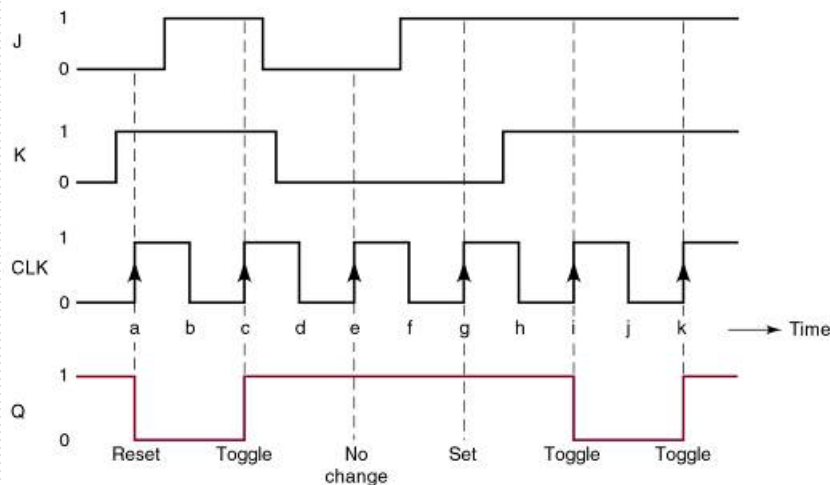

Clocked J-K Flip-Flop

- Negative Edge Triggering

 Clocked J-K flip-flop that responds only to the negative edge of the clock.




J	K	CLK	Q
0	0	↓	Q_0 (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	\bar{Q}_0 (toggles)

Clocked J-K Flip-Flop

- Logic Diagram

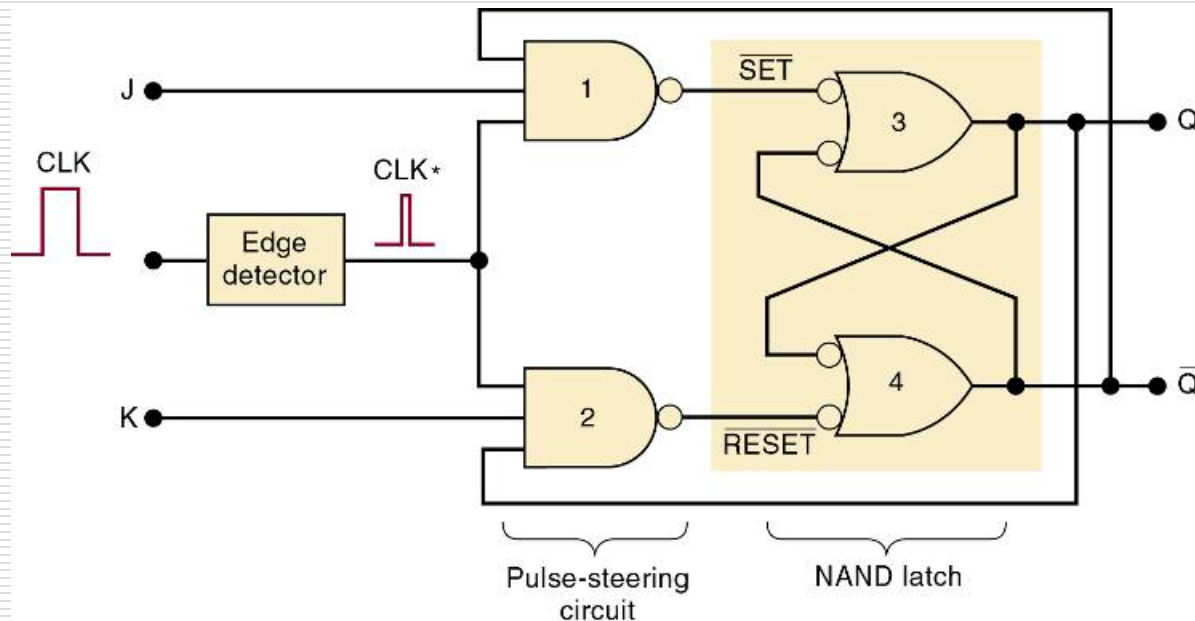
- The internal circuitry of an edge-triggered J-K flip-flop contains the same three sections as the edge-triggered S-R flip-flop.



Clocked D (Data) Flip-Flop

- ❑ One data input (D)
- ❑ output (Q) changes to the value of the input at either the positive- or negative-going clock trigger.
- ❑ can be implemented with a J-K FF by tying the J input to the K input through an inverter.
 - The same can be done to convert the S-R flip-flop to a D flip-flop
- ❑ Useful for parallel data transfer.

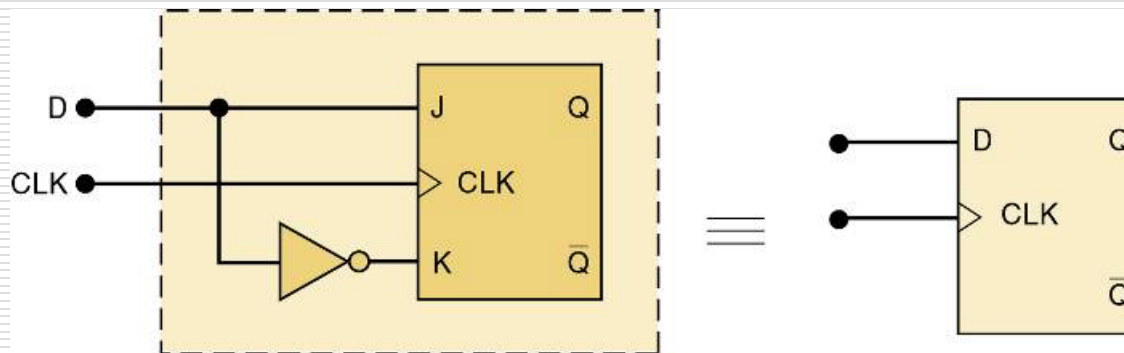
Positive Edge-triggered D flip-flop implementation from a J-K flip-flop.



Clocked D Flip-Flop

- Positive Edge Triggering

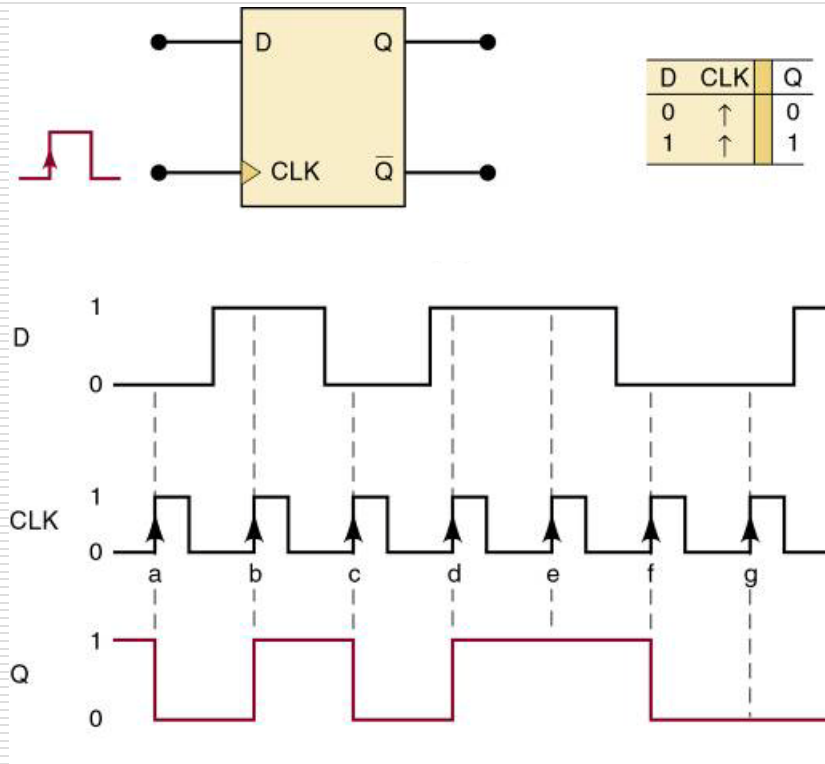
D flip-flop that triggers only on positive-going transitions.



Clocked T (Toggle) Flip-Flop

- Positive Edge Triggering

 An edge-triggered T flip-flop is easily implemented by connecting J and K inputs together in an edge-triggered J-K flip-flop.



When $T=0$ ($J=K=0$), a clock edge does not change the output.
When $T=1$ ($J=K=1$), a clock edge complements the output.

Flip-Flops - Summary

- Characteristic Tables/Equations

Characteristic Tables

SR Flip-flop

S	R	Q (t+1)	
0	0	Q (t)	No change
0	1	0	RESET
1	0	1	SET
1	1	?	Undefined

J/K Flip-Flop

J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Characteristic Equations

SR Flip-flop:

$$Q(t+1) = S + R' Q(t)$$

JK Flip-flop:

$$Q(t+1) = JQ'(t) + K'Q(t)$$

D Flip-flop:

$$Q(t+1) = D$$

T Flip-flop:

$$Q(t+1) = T \oplus Q(t)$$

D Flip-Flop

D	Q(t + 1)	
0	0	Reset
1	1	Set

T Flip-Flop

T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement

Flip-Flops - Summary

- Excitation Tables

Excitation Tables

SR Flip-flop

$Q(t)$	$Q(t+1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

D Flip-flop

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

J-K Flip-flop

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


T Flip-flop

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Asynchronous Inputs

- Most clocked FFs also have one or more asynchronous inputs which operate independently of the synchronous inputs and clock input.
- Asynchronous inputs can be used to override all the other inputs in order to place the FF in one state or the other at any time.
- IC manufacturers do not agree on nomenclature for asynchronous inputs.
 - The most common designations are *PRE* (PRESET) and *CLR* (CLEAR).
 - Labels such as *S-D* (direct SET) and *R-D* (direct RESET) are also used.

 Clocked J-K flip-flop with asynchronous inputs.




J	K	Clk	$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	Q
0	0	↓	1	1	Q (no change)
0	1	↓	1	1	0 (Synch reset)
1	0	↓	1	1	1 (Synch set)
1	1	↓	1	1	\bar{Q} (Synch toggle)
x	x	x	1	1	Q (no change)
x	x	x	1	0	0 (asynch clear)
x	x	x	0	1	1 (asynch preset)
x	x	x	0	0	(Invalid)


Asynchronous Inputs

 - Example

A J-K FF that responds to a NGT on its clock input and has active-LOW asynchronous inputs



Point	Operation
a	Synchronous toggle on NGT of CLK
b	Asynchronous set on $\overline{PRE} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{CLR} = 0$
f	CLR overrides the NGT of CLK
g	Synchronous toggle

 


Flip-Flop Applications

- Examples of applications:
 - Storing binary data
 - Transferring binary data between locations
 - Synchronization
 - Frequency Division and Counting
-

Flip-flop Applications

- An example (Synchronous Data Storage and Transfer)

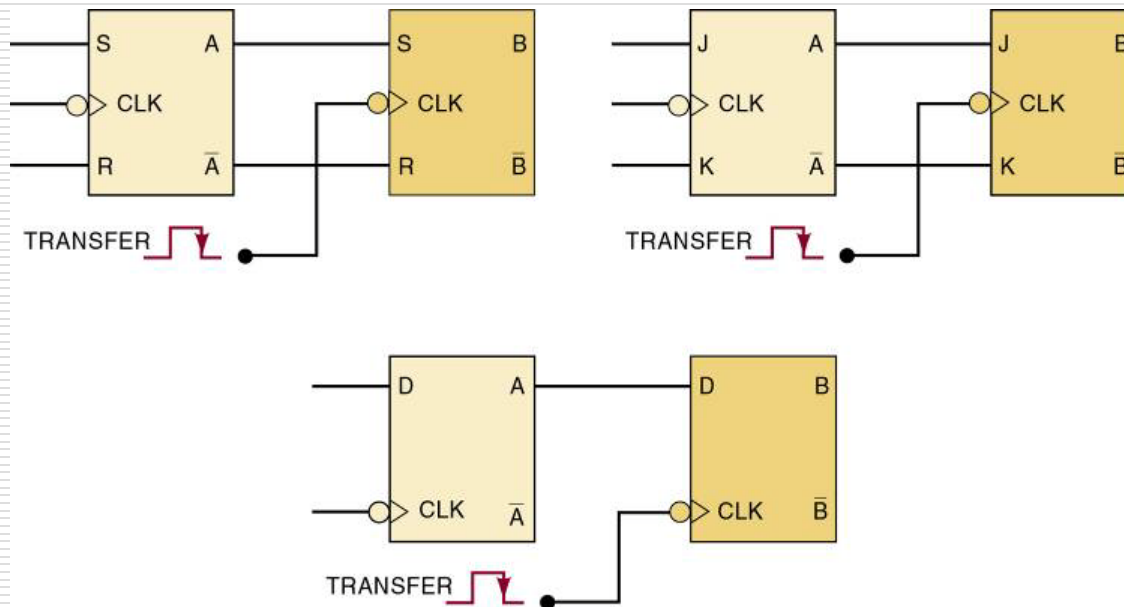Synchronous data transfer operation by various clocked FFs.




CLK inputs are used to perform the transfer.

Flip-flop Applications

- An example (Parallel Data Storage and Transfer)

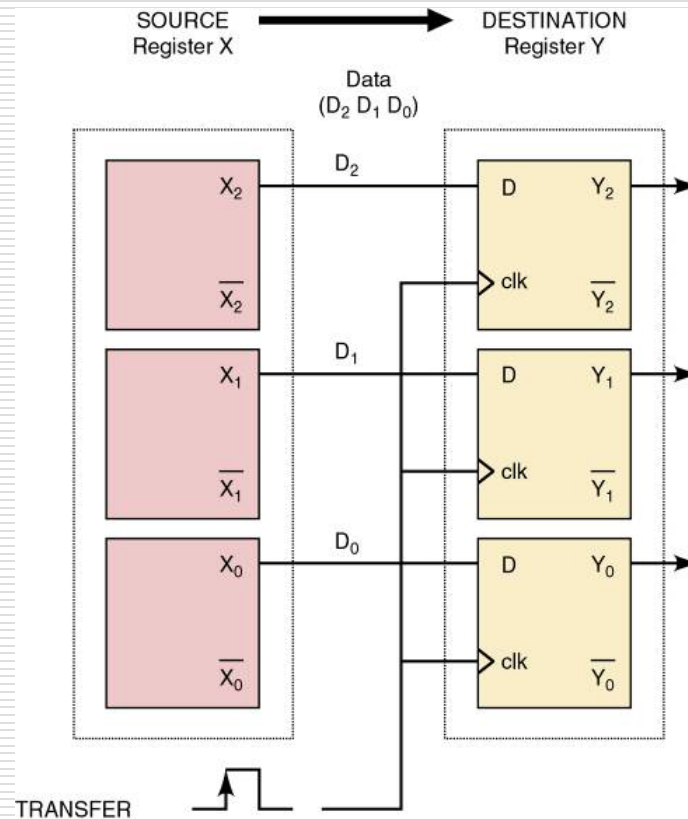
Transferring the bits of a register *simultaneously* is a *parallel* transfer.



Flip-flop Applications

- An example (Microcomputer application)

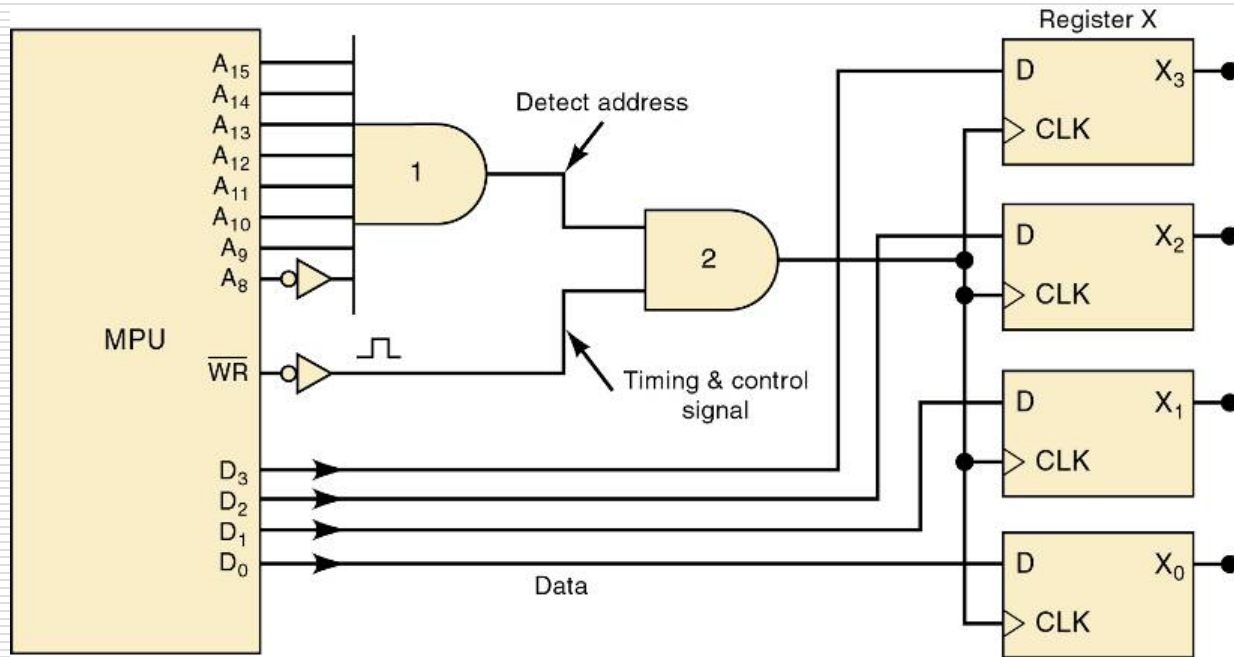Microprocessor transferring binary data to an external register



- ❑ Microprocessor units (MPUs) perform many functions involving use of registers for data transfer and storage.

Finite State Machines

- * Mealy and Moore Models
 - Block Diagram
 - State Diagram- Example
 - State Table - Example

Finite State Machines

- Mealy and Moore Models

□ Sequential Circuits or Sequential Machines are also called *Finite State Machines* (FSMs). Two formal models exist:

■ Mealy Model

- Named after G. Mealy
- Outputs are a function of **inputs** and **present states**
- Usually specified on the state transition arcs.


■ Moore Model

- Named after E.F. Moore
 - Outputs are a function of ONLY **present states**
 - Usually specified on the states.
-

Finite State Machines

- Mealy and Moore Models

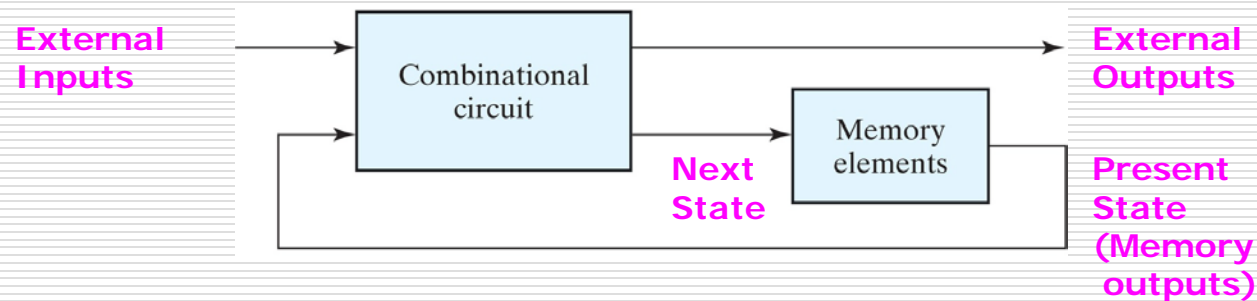➤ Block Diagram of a Sequential Logic Circuit



Next state function

Next State = $f(\text{Inputs}, \text{Present State})$

Output function (Mealy)

Outputs = $g(\text{Inputs}, \text{Present State})$



Output function (Moore)

Outputs = $h(\text{Present State})$

Output function type depends on specification and affects the design significantly

Finite State Machines

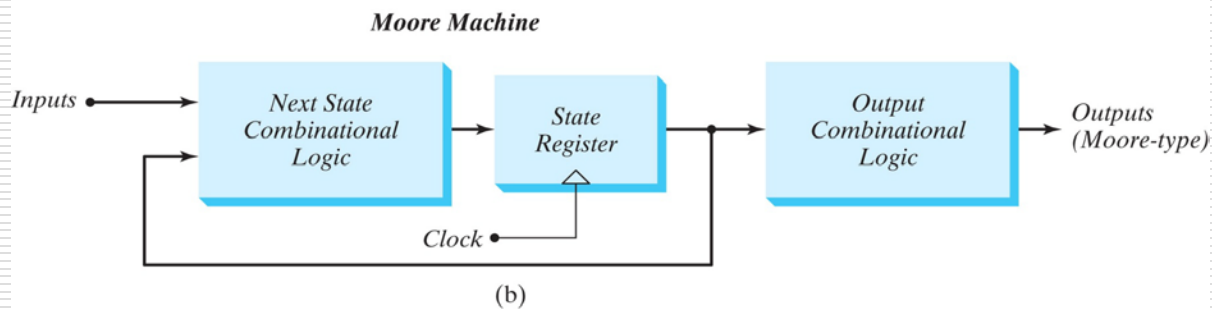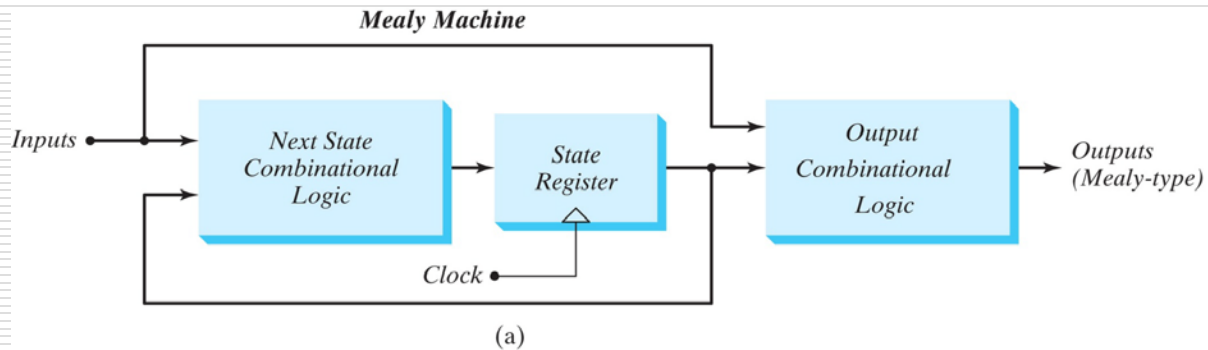
- Mealy and Moore Models (Block Diagrams)




Finite State Machines

- Mealy and Moore Models (Example State Diagrams)

 - Mealy Model State Diagram
maps **inputs and state** to **outputs**



 
- Moore Model State Diagram
maps **states** to **outputs**



Finite State Machines


- Mealy and Moore Models (Example State Tables)

 - Mealy Model state table maps inputs and state to outputs



Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

 - Moore Model state table maps state to outputs



Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

References

Slides adopted from the books

- ❑ Ronald J.Tocci, Neal S.Widmer, and Gregory L.Moss, "Digital Systems- Principles and Application"- 10th Edition, Pearson Education International, 2007
- ❑ M.Morris Mano and Michael D. Ciletti, " Digital Design," 5th Edition, Pearson Education International, 2012
- ❑ M.Morris Mano and Charles R. Kime, " Logic and Computer Design Fundamentals," 4th Edition, Pearson Education International, 2008
- ❑ Thomas L.Floyd, "Digital Fundamentals," 10th Edition, Pearson Education International, 2009